


Modeling and simulation of three electrical circuits

Emanuel Cruvinel

Overview

- ▶ We'll be modeling three electrical circuits using Simscape® (Simulink package)
- ▶ All the circuits may have a DC voltage source, DC current source, resistors, capacitances and inductors.
- ▶ Current and voltage will be measured on each circuit component.


First model

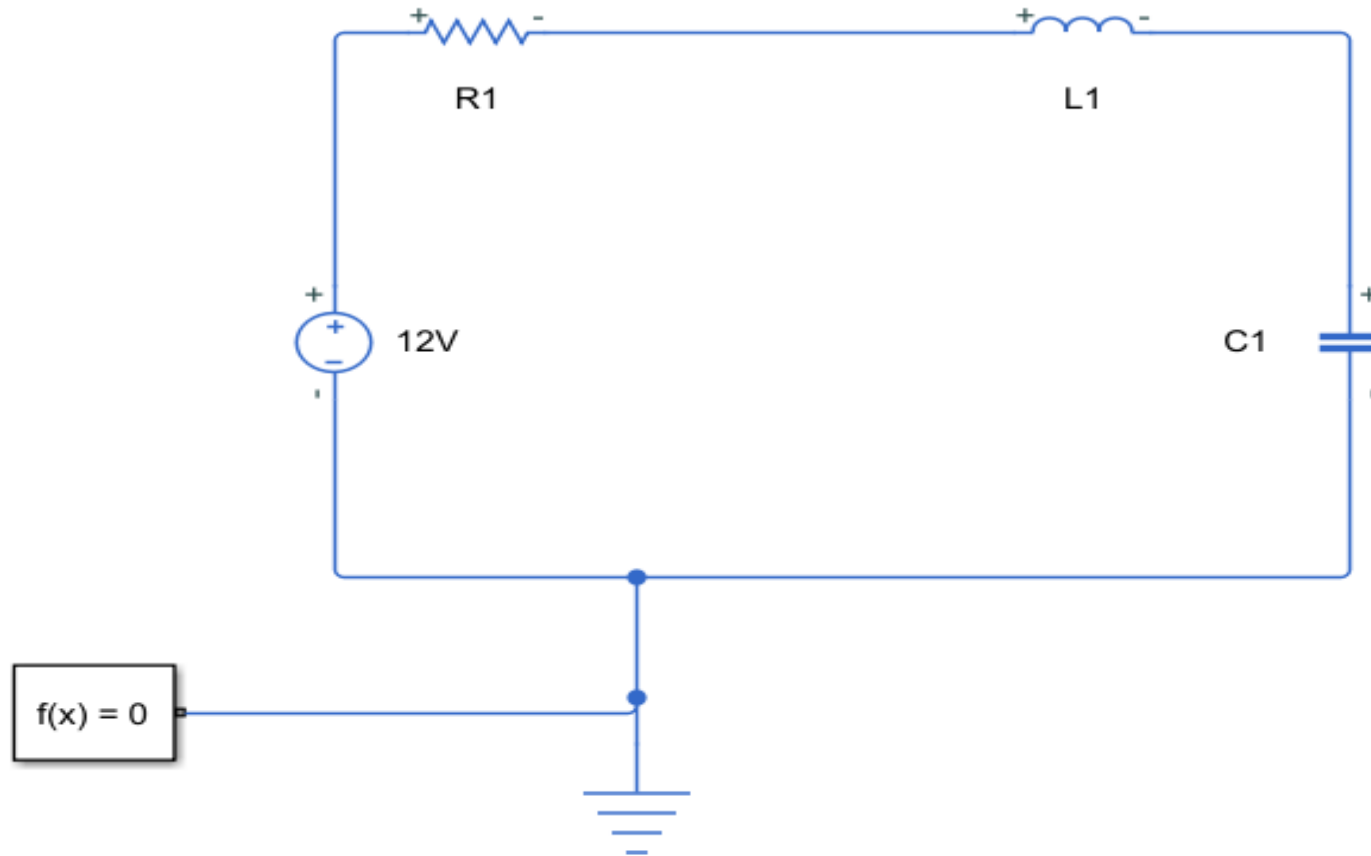


Input parameters

- ▶ $R1 = 1 \text{ ohm}$
- ▶ $C1 = 1 \text{ }\mu\text{F}$
- ▶ $L1 = 1 \text{ }\mu\text{H}$
- ▶ DC Voltage Source = 12 V
- ▶ Simulation time = $1.2\text{e-}6$ seconds


Results: Current (A)

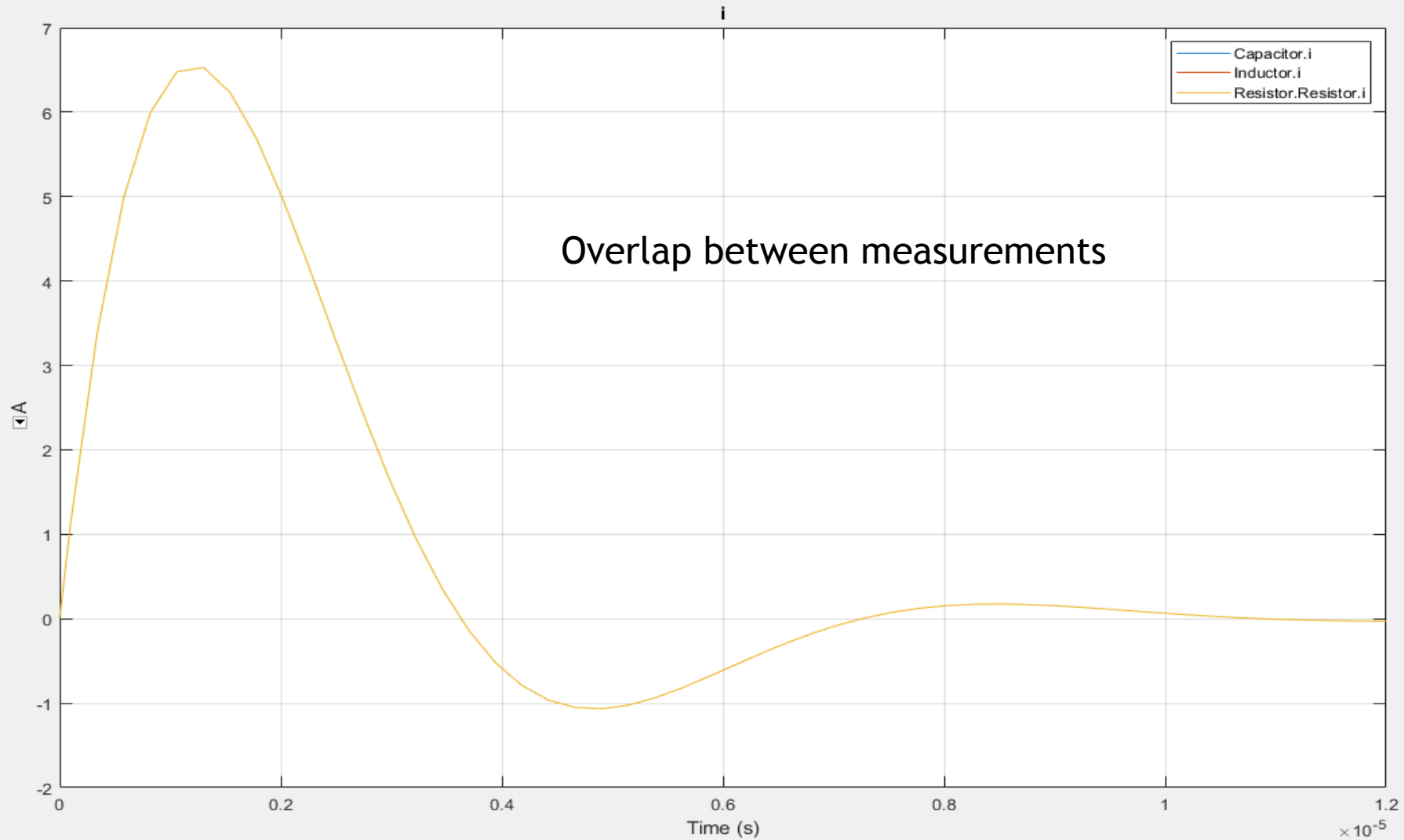

Results: Voltage (V)

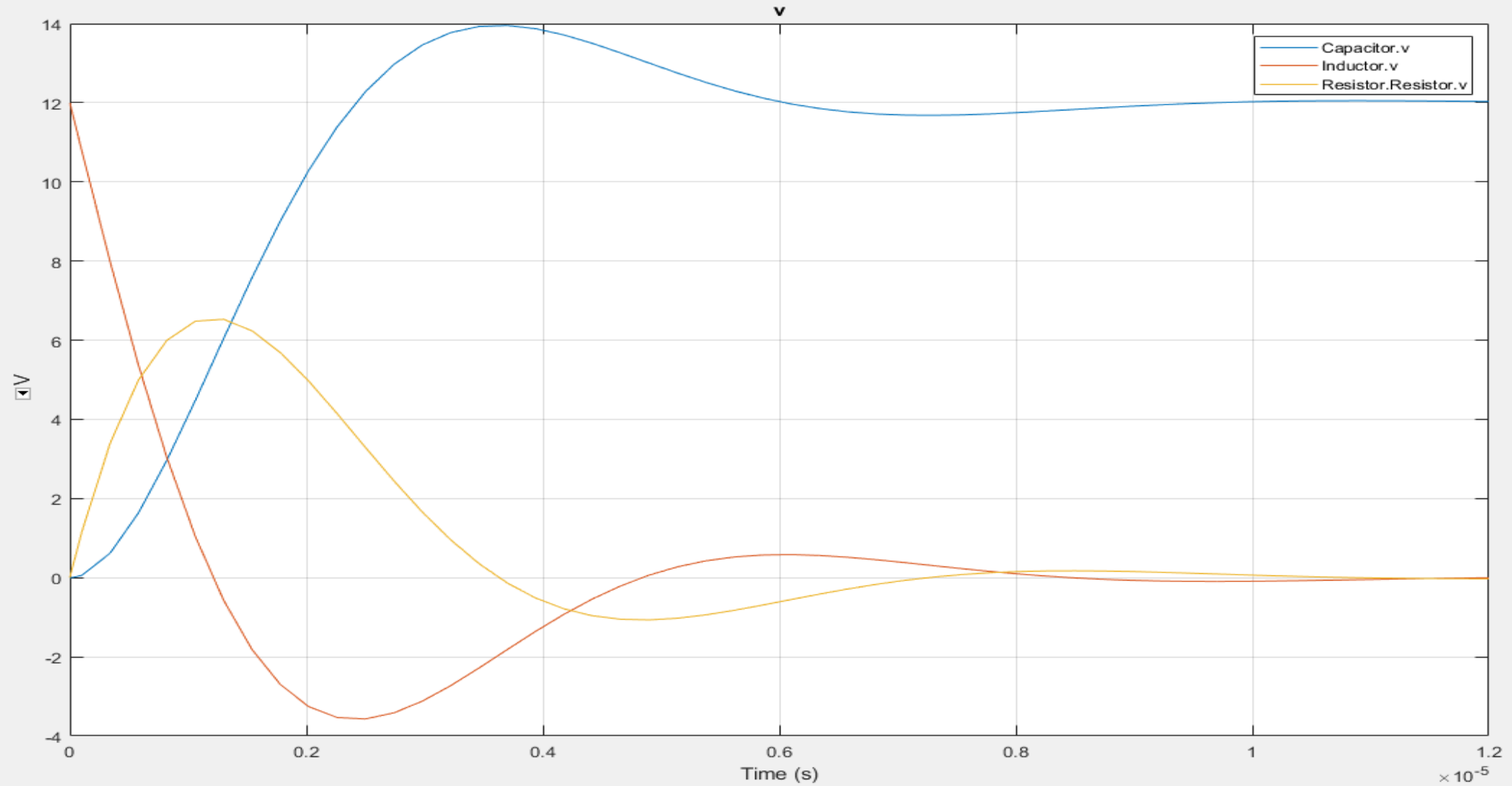


Second model

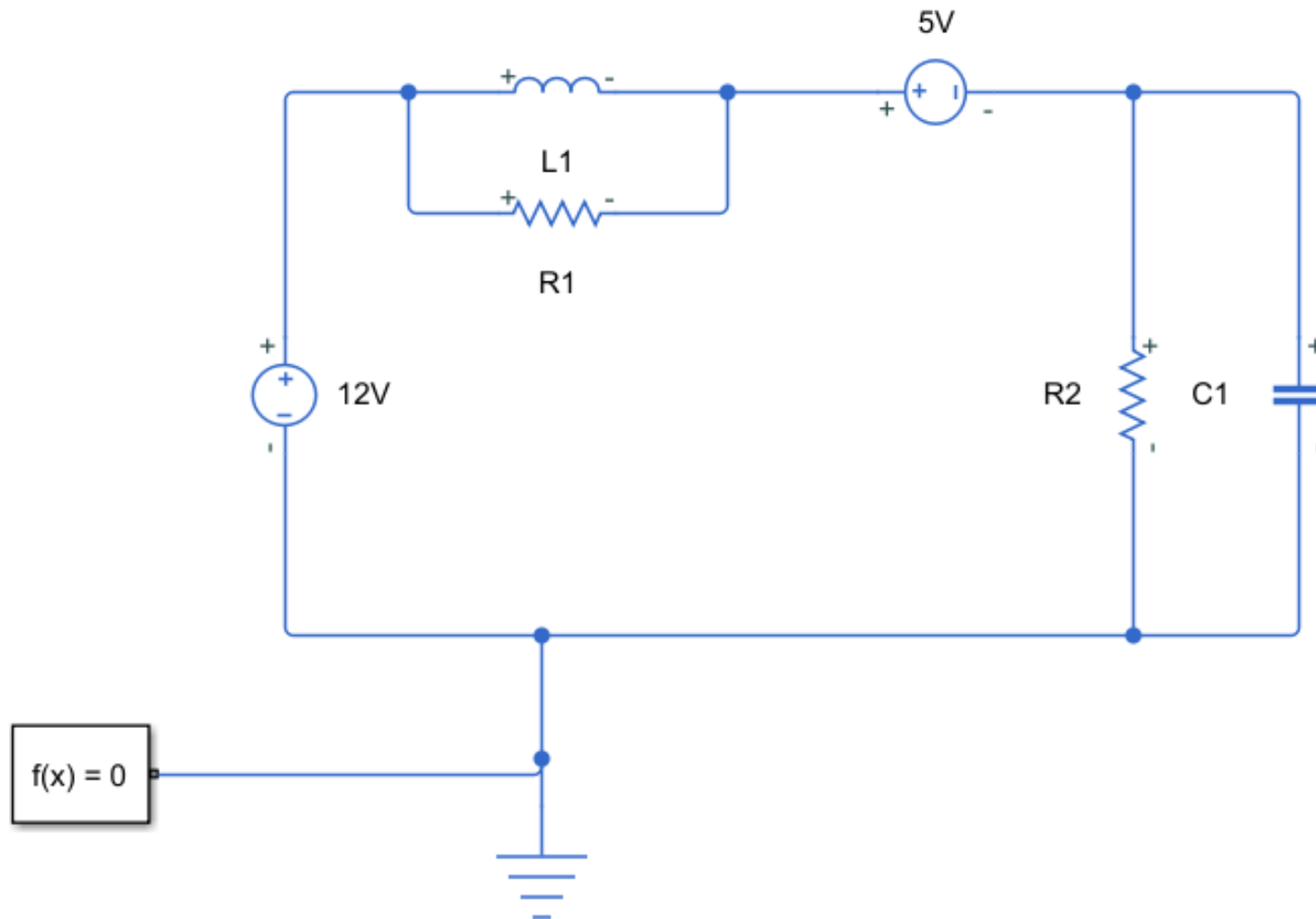


Input parameters

- ▶ $R1 = 1 \text{ ohm}$
- ▶ $R2 = 5 \text{ ohms}$
- ▶ $C1 = 1 \text{ }\mu\text{F}$
- ▶ $L1 = 1 \text{ }\mu\text{H}$
- ▶ DC Voltage Source 1 = 12 V
- ▶ DC Voltage Source 2 = 5 V
- ▶ Simulation time = $1.2\text{e-}5$ seconds


Results: Voltage (V)

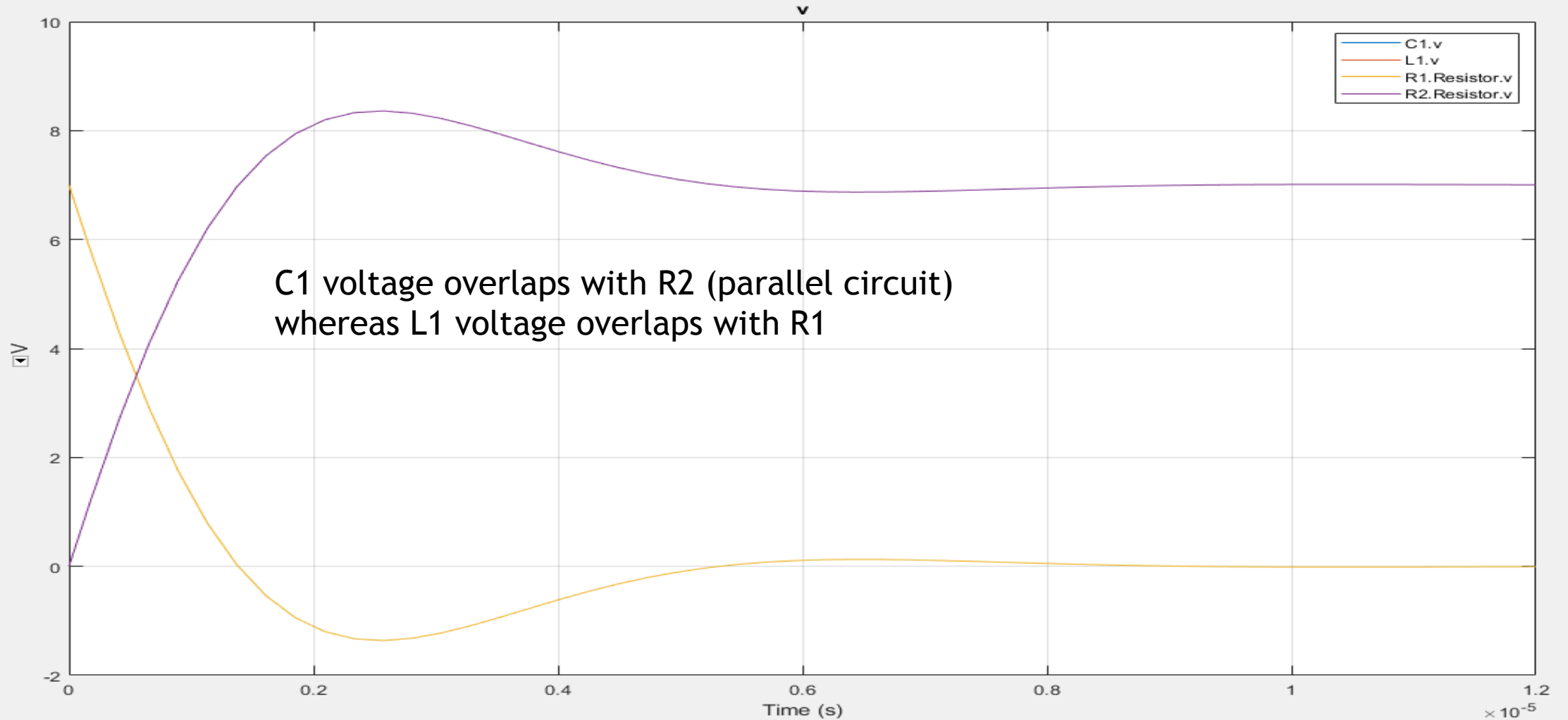

Results: Current (A)

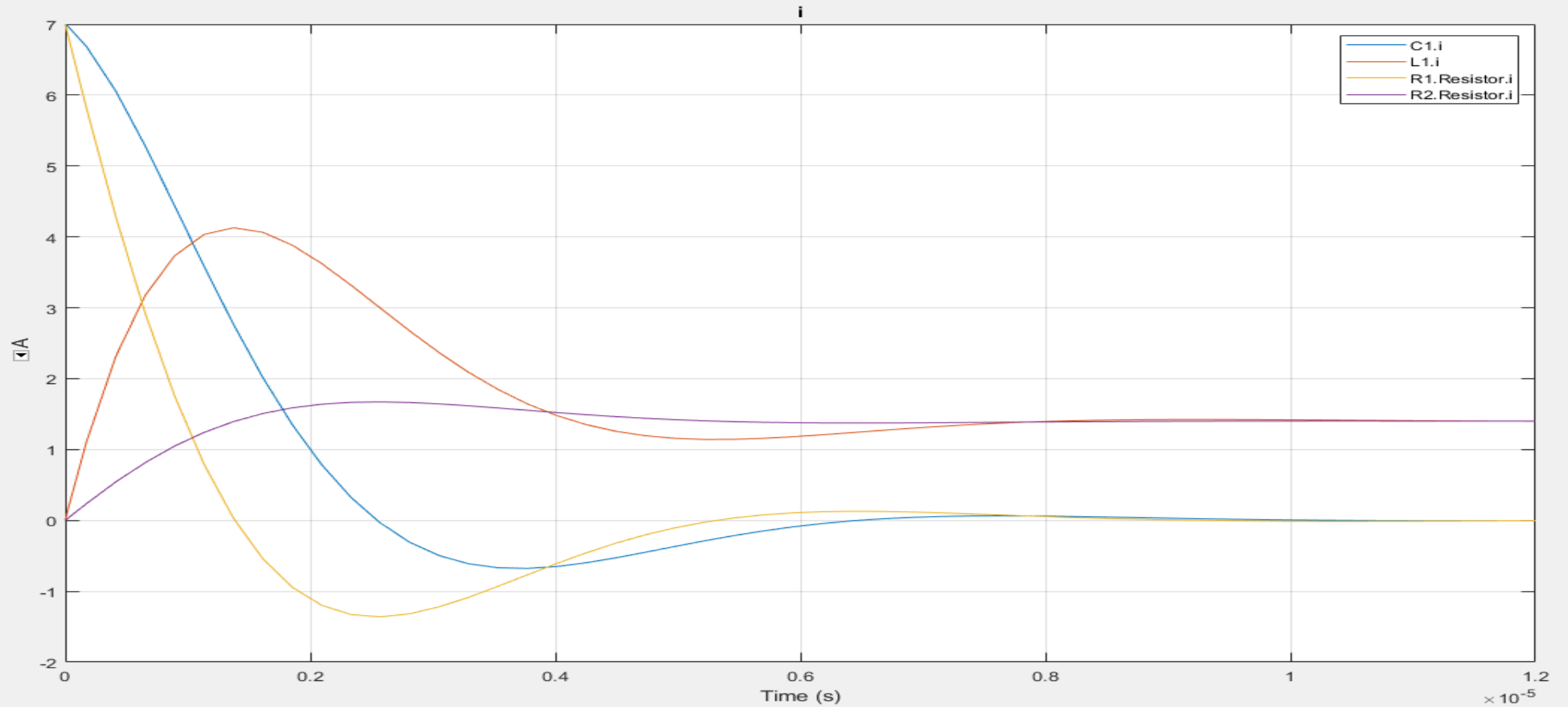



Third Model

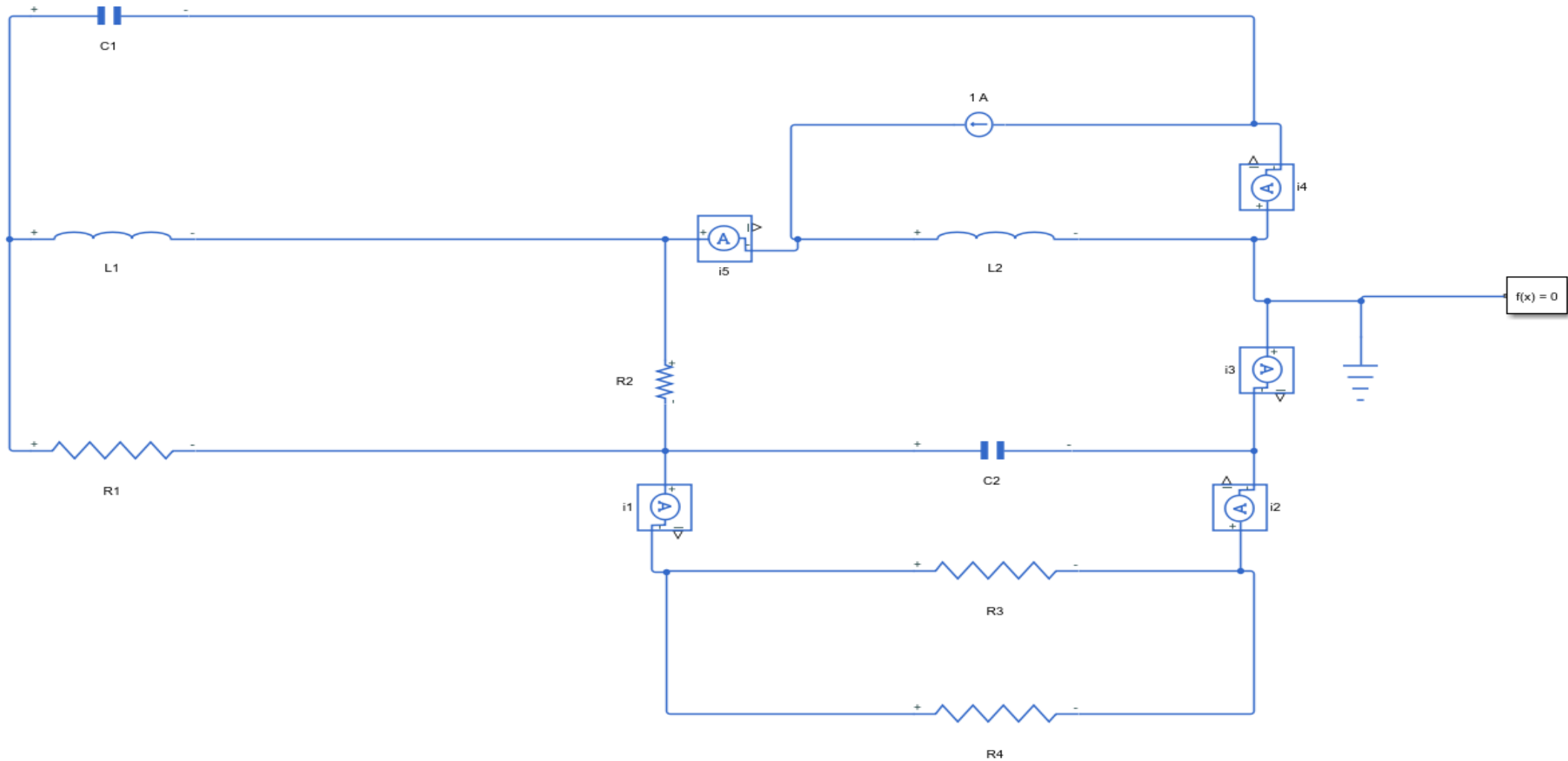



Input parameters

- ▶ $R1 = 1 \text{ ohm}$
- ▶ $R2 = 2 \text{ ohms}$
- ▶ $R3 = 3 \text{ ohms}$
- ▶ $R4 = 4 \text{ ohms}$
- ▶ $C1 = 1 \text{ }\mu\text{F}$
- ▶ $C2 = 2 \text{ }\mu\text{F}$
- ▶ $L1 = 1 \text{ }\mu\text{H}$
- ▶ $L2 = 2 \text{ }\mu\text{H}$
- ▶ DC Current Source = 1 A
- ▶ Simulation time = $7\text{e-}5$ seconds

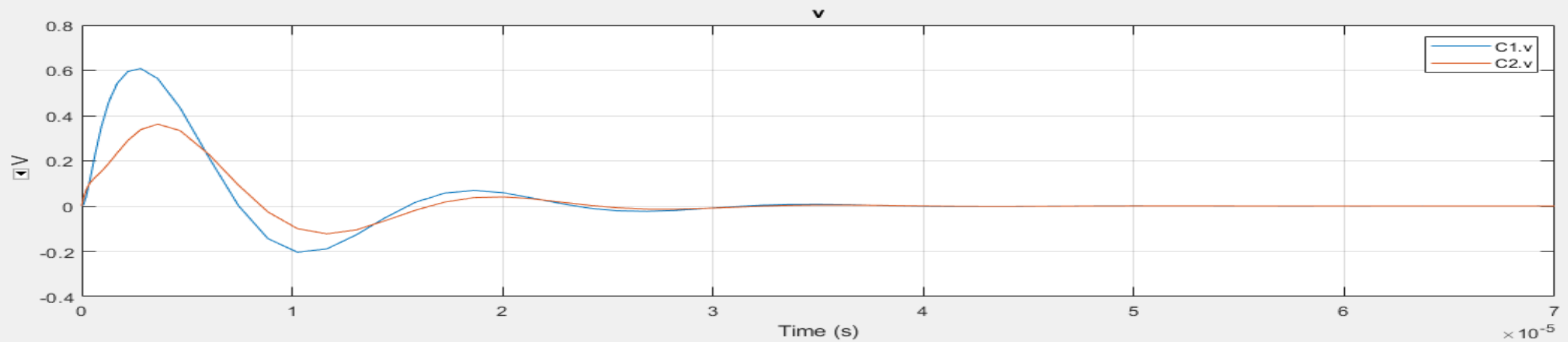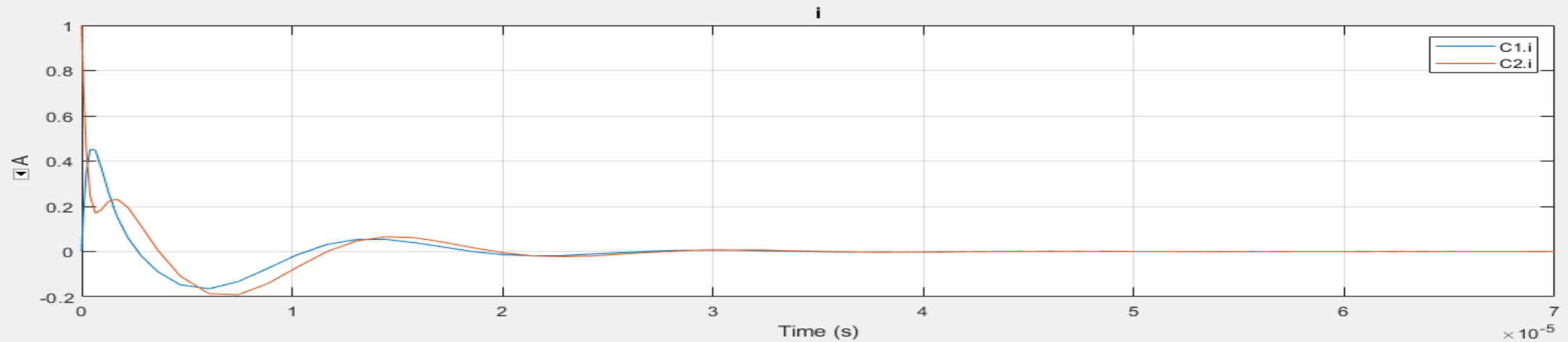
Results: Current (A) and Voltage (V) on Capacitors



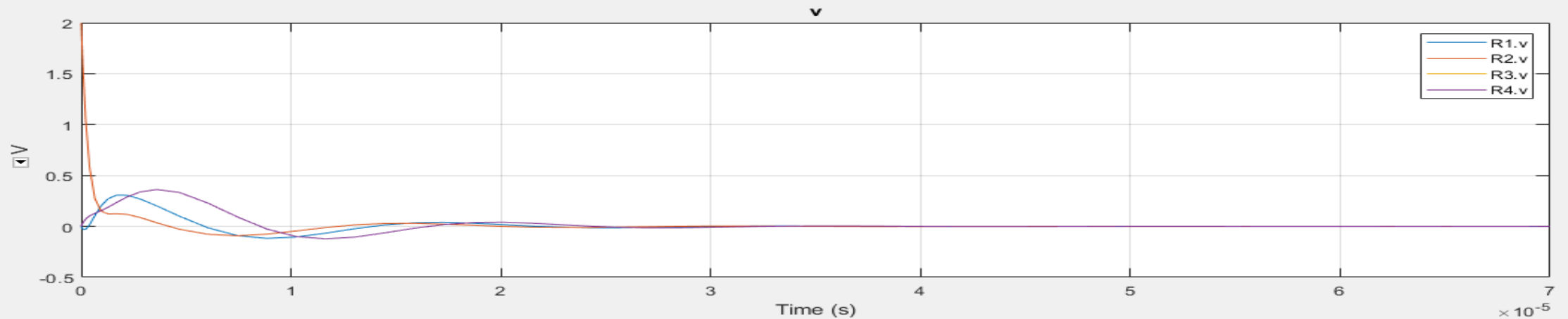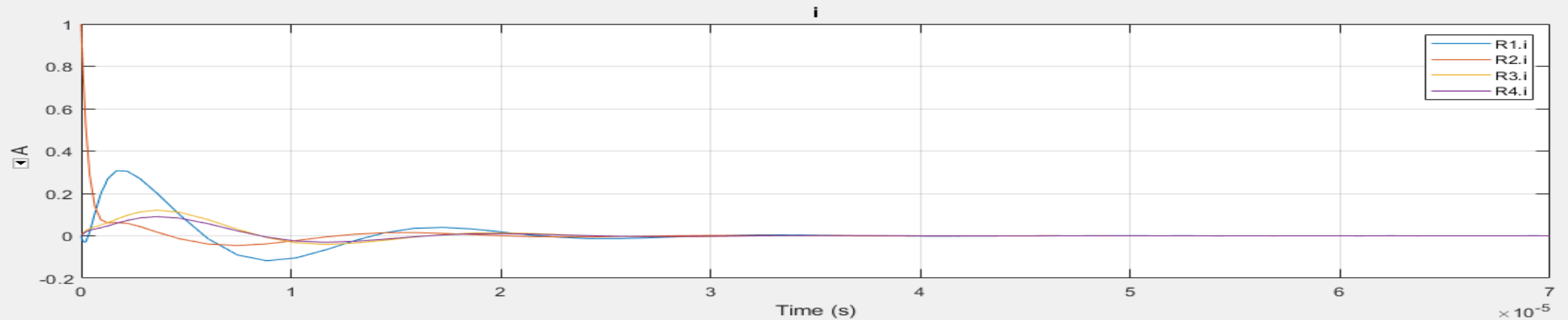
Results: Current (A) and Voltage (V) on Resistors



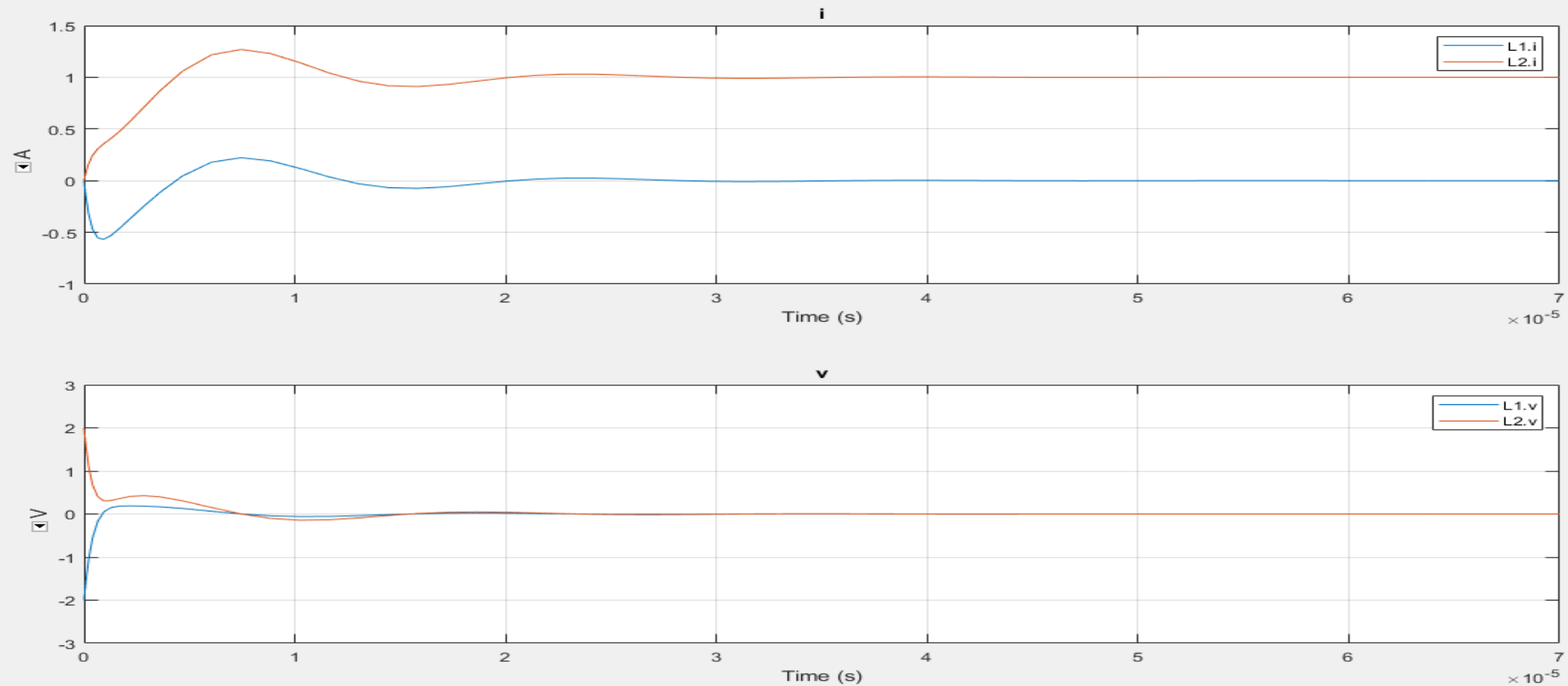Results: Current (A) and Voltage (V) on Inductors



Results: Current i1 to i5 (A)

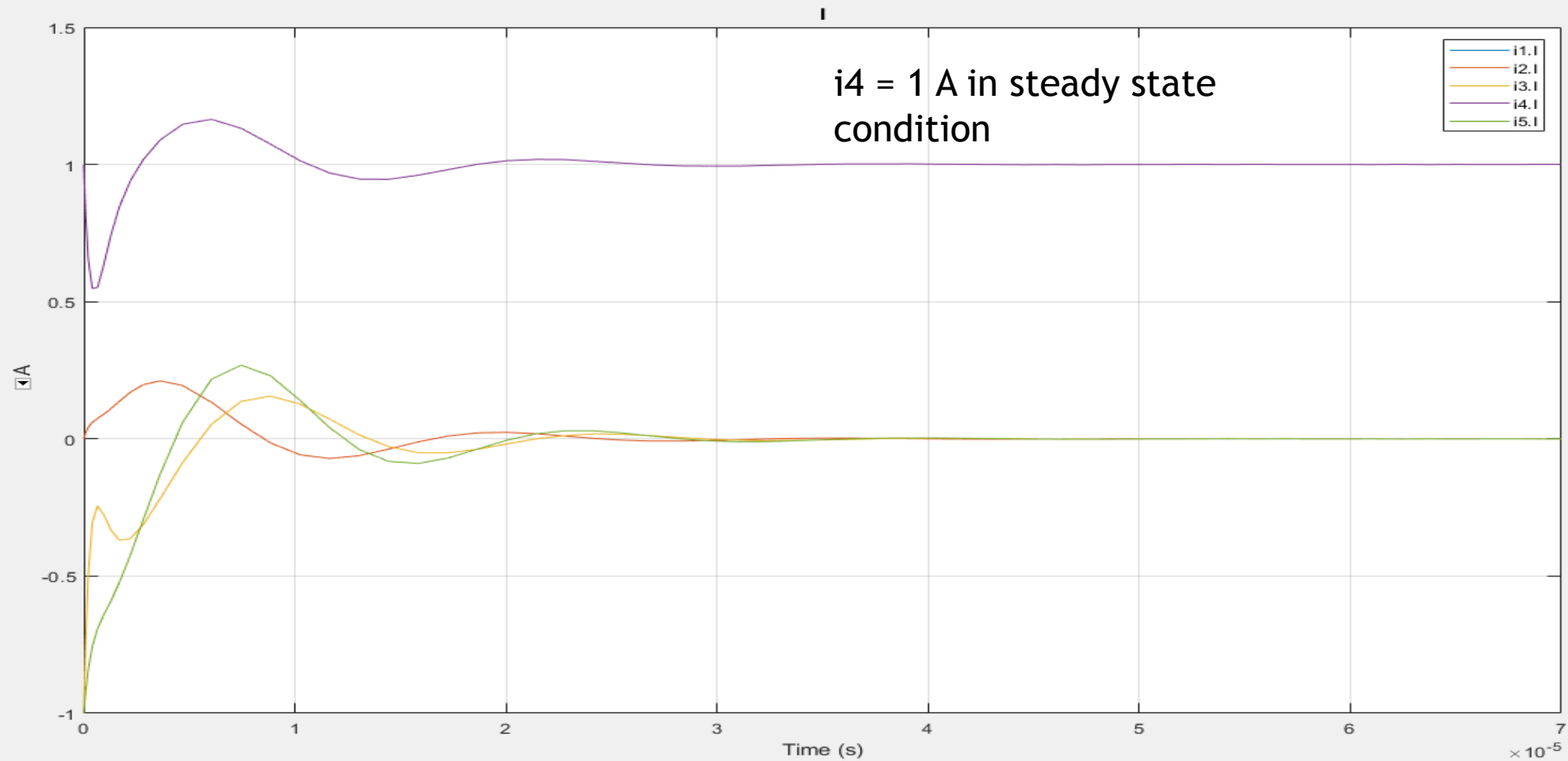

Conclusions

- ▶ All three electrical circuits were modeled using Simscape®
- ▶ The results are in agreement with RLC circuit theory